


*Electric Circuits I*

*DC Circuits*

*Midterm Revision (2)*

1

Final (2014)

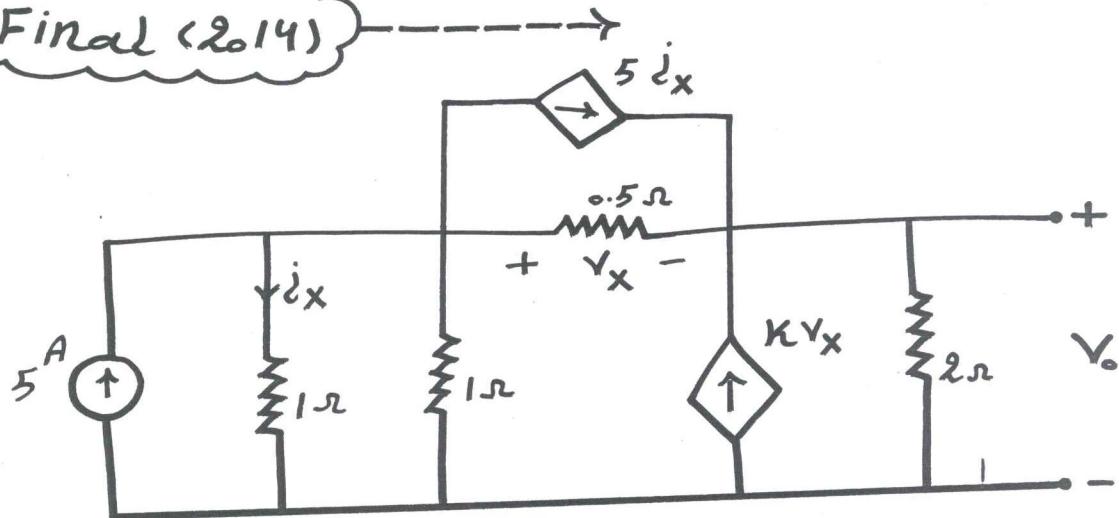


→ For the shown circuit, find the value of  $K$  so that the output voltage  $V_o = 2V$ .

← {solution} →

$$\text{Let } i_2 = KV_x$$

$i_1$  in  $\parallel$  in → equal and parallel

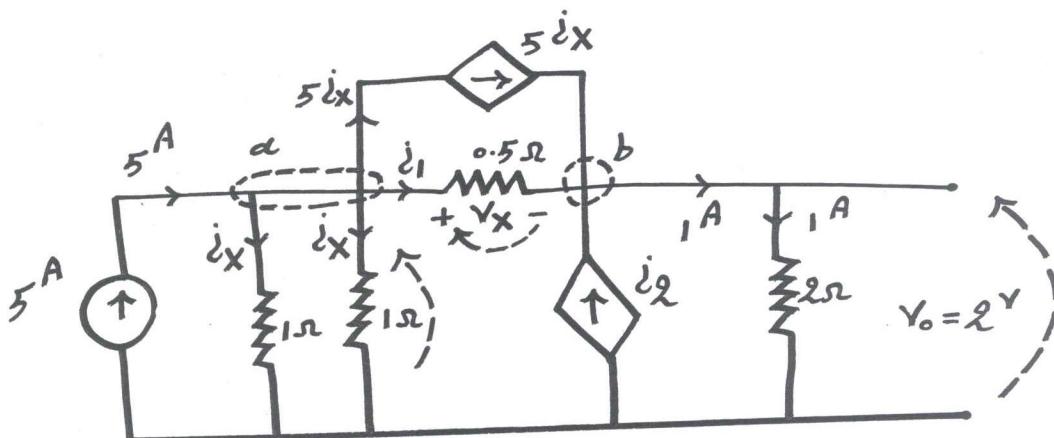resistors → the same  
current will pass through  
them.



Let  $i_1$  → assumed current.

$\rightarrow$  using KCL and KVL:

2

$\rightarrow$  KCL at node (a):

$$\therefore 5 = i_x + i_x + 5 i_x + i_1$$

$$\therefore 7 i_x + i_1 = 5 \rightarrow 1$$

$\rightarrow$  KCL at node (b):

$$\therefore 1 = i_1 + i_2 + 5 i_x$$

$$\therefore 5 i_x + i_1 + i_2 = 1 \rightarrow 2$$

$\rightarrow$  KVL : (1\Omega + 0.5\Omega + 2\Omega) loop:

$$\therefore (1) i_x - 0.5 i_1 - 2 = 0$$

$$\therefore i_x - 0.5 i_1 = 2 \rightarrow 3$$

solving 1, 2 and 3

$$\therefore i_x = 1^A$$

$$\therefore i_1 = -2^A$$

$$\therefore i_2 = -2^A$$

3

$$\hookrightarrow V_x = 0.5(i_1)$$

$$= 0.5(-2) = -1^V$$


$$\hookrightarrow i_2 = K V_x$$

$$\therefore -2 = K (-1)$$

$\therefore K = 2$

$\hookrightarrow$  another method:

→ using nodal analysis:

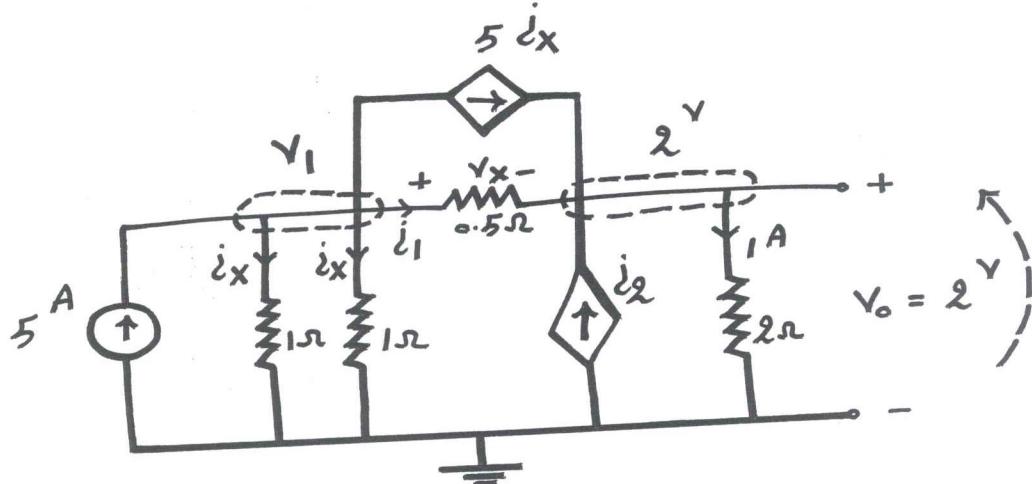

KCL at node (1)

$$\therefore i_x + i_x + 5i_x + \frac{V_1 - 2}{0.5} = 5$$

$$\hookrightarrow i_x = \frac{V_1}{1} = V_1$$

$$\therefore 7V_1 + 2V_1 - 4 = 5$$

$$\therefore 9V_1 = 9$$

4

$$\therefore V_1 = 1^V$$

$$\therefore i_X = 1^A$$

$$\therefore i_1 = \frac{V_1 - 2}{0.5} = \frac{1 - 2}{0.5} = -2^A$$

$$\therefore V_X = 0.5 i_1 = 0.5 (-2) = -1^V$$

KCL at node 2

$$\therefore 5i_X + i_1 + i_2 = 1$$

$$\therefore 5(1) + (-2) + i_2 = 1$$

$$\therefore 3 + i_2 = 1$$

$$\therefore i_2 = -2^A$$


$$\therefore i_2 = K V_X$$

$$\therefore -2 = K(-1)$$

$\therefore K = 2$

Final (2014) ----->


5

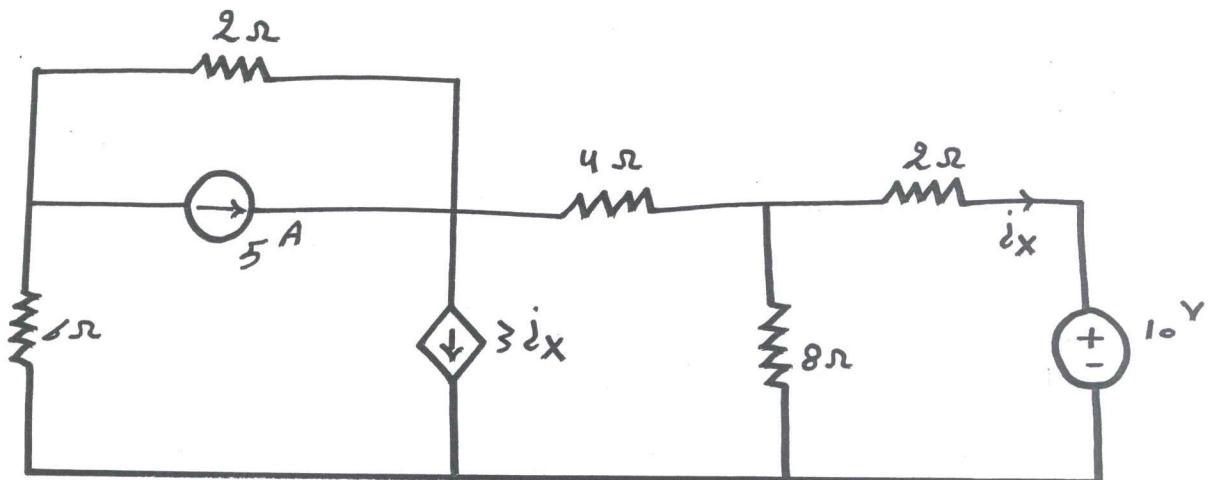

use source transformation to find  $i_x$  in the shown circuit. Then find the power of each source.

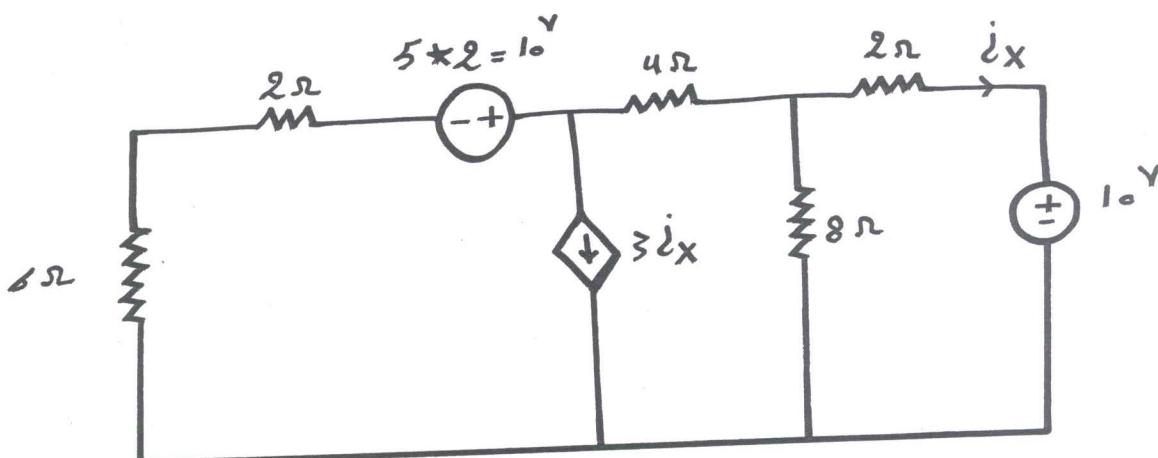
**Solution**

$\rightarrow 5A \parallel 2\Omega \rightarrow$  source transformation:




$\rightarrow 6 + 2 = 8\Omega \rightarrow$  series with  $10V$  source:


6

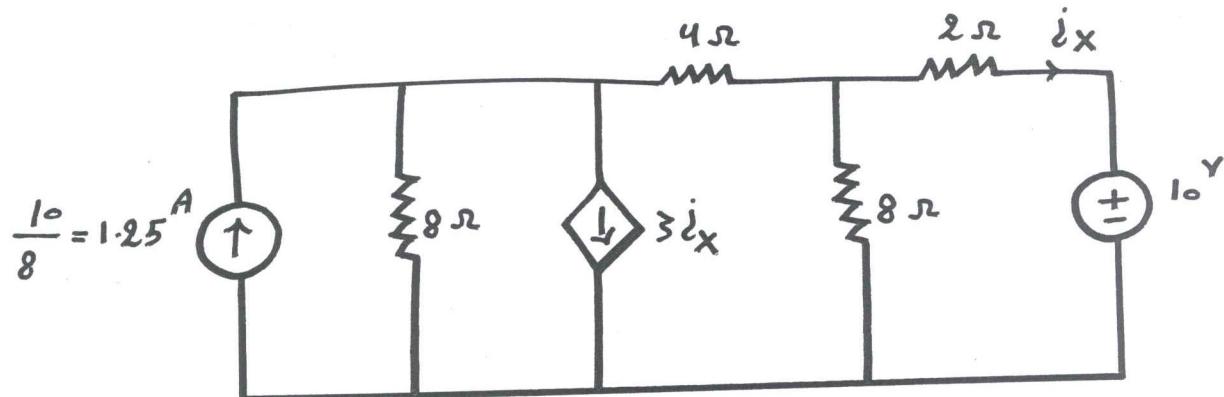

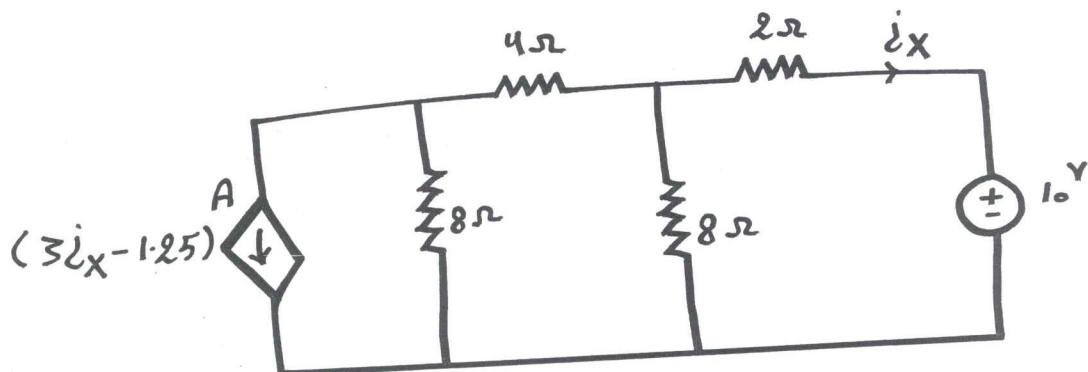$\hookrightarrow 1.25 \text{ A}, 3j_x \text{ A} \rightarrow$  parallel current sources:




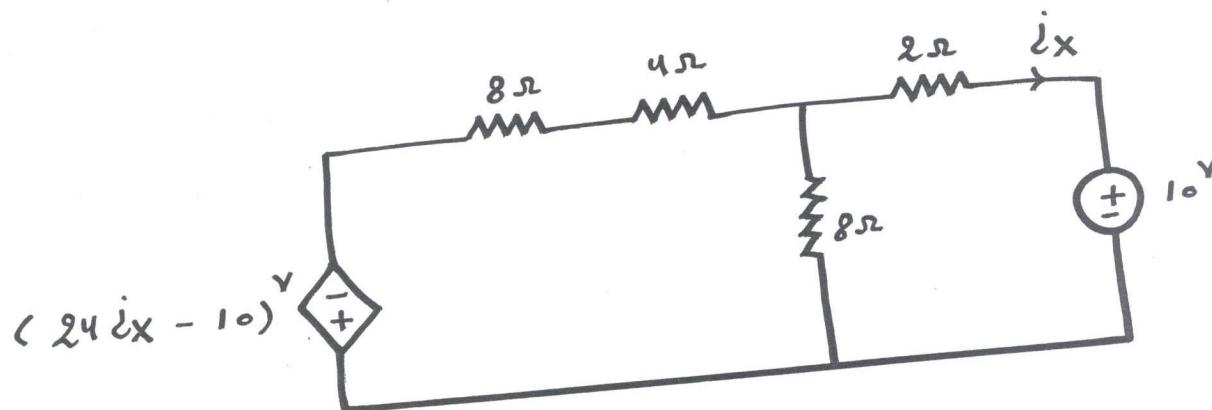$\hookrightarrow (3j_x - 1.25) \text{ A} \parallel 8 \Omega \rightarrow$  source transformation:




$\hookrightarrow 8 + 4 = 12 \Omega \rightarrow$  series with  $(24j_x - 10) \text{ V}$  source:

27

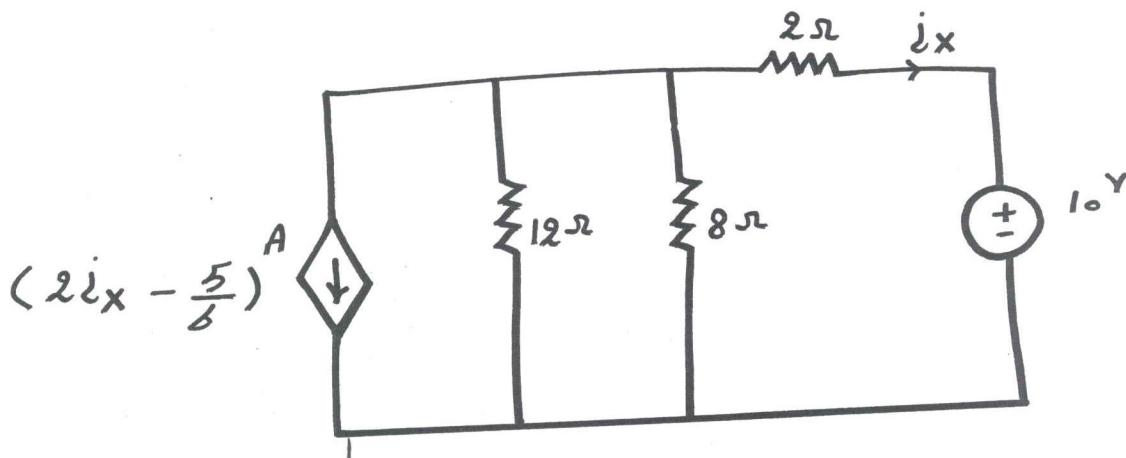

$$\hookrightarrow 12 \parallel 8 = \frac{12 \times 8}{12 + 8} = 4.8 \Omega$$

$\hookrightarrow (2j_x - \frac{5}{8})^A \parallel 4.8 \Omega \rightarrow$  source transformation:

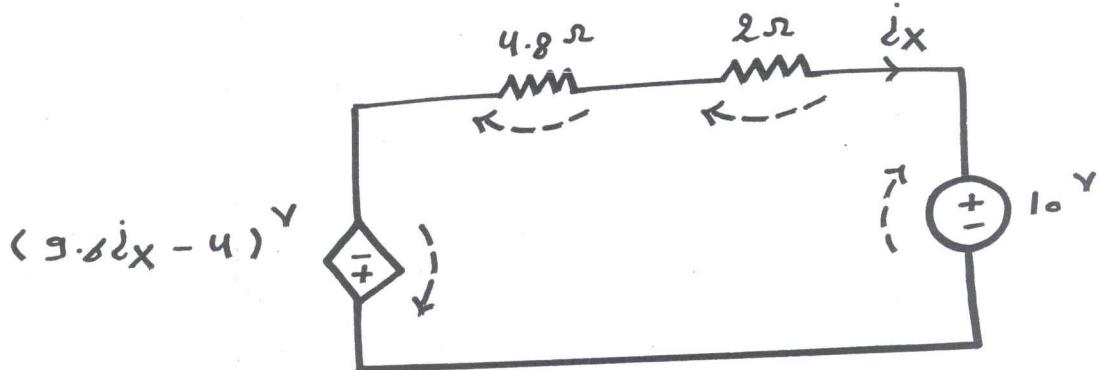KVL


$$\therefore 9.6 j_x - 4 + 10 + 2 j_x + 4.8 j_x = 0$$

$$\therefore 16.4 j_x = -4$$

$$\therefore j_x = -\frac{15}{41} A = -0.366 A$$

↳ Find the Power of each source:

→ back to the original circuit:

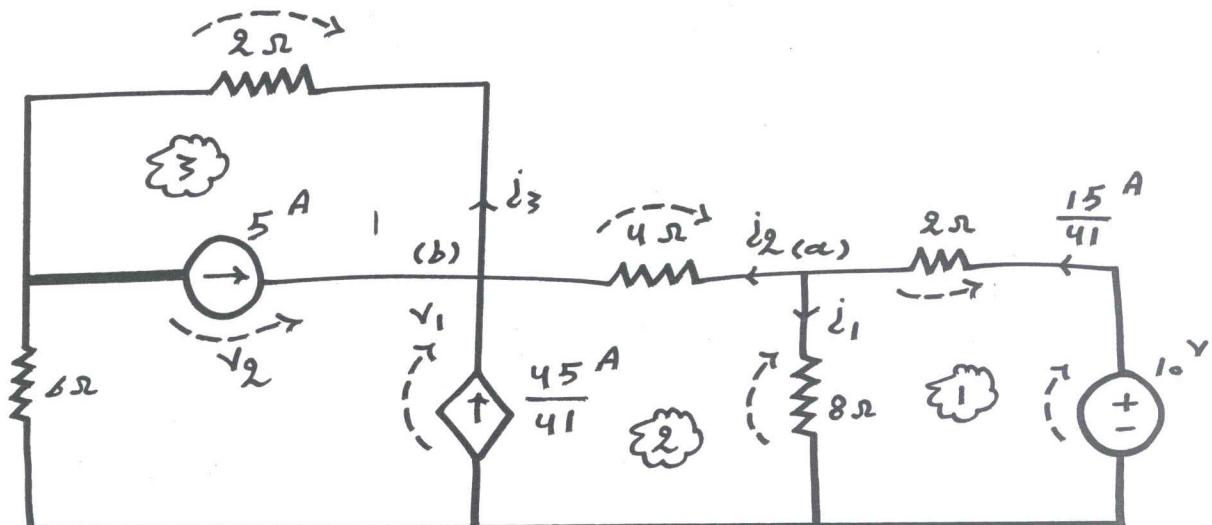

$$\text{↳ } P_{10V} = 10V \times \frac{15}{41}$$

$$\therefore P_{10V} = \frac{150}{41} W = 3.66 W$$

Generated Power

KVL : Loop (1) :

$$\therefore 8i_1 + 2\left(\frac{15}{41}\right) - 10 = 0$$

$$\therefore 8i_1 = 10 - \frac{30}{41}$$

$$\therefore i_1 = \frac{95}{82} A$$

KCL : (a) :

$$\therefore i_2 = \frac{15}{41} - i_1 = -\frac{65}{82} A$$

9

KVL : Loop 2 :

$$\therefore v_1 + 4j_2 - 8j_1 = 0$$

$$\therefore v_1 = 8j_1 - 4j_2$$

$$= 8\left(\frac{95}{82}\right) - 4\left(-\frac{65}{82}\right)$$

$$= \frac{510}{41} V$$

$$\therefore P_{\text{Generated}} = \frac{510}{41} V \times \frac{45}{41} = 13.65 W$$

dependent  
sourceGenerated PowerKCL : (b) :

$$\therefore j_3 = 5 + \frac{45}{41} + j_2$$

$$= 5 + \frac{45}{41} - \frac{65}{82}$$

$$= \frac{435}{82} A$$

KVL : Loop 3 :

$$\therefore v_2 = 2j_3 = 2\left(\frac{435}{82}\right) = \frac{435}{41} V$$


$$\therefore P_{5A} = \frac{435}{41} V \times 5 A = 53.049 W$$

Generated Power

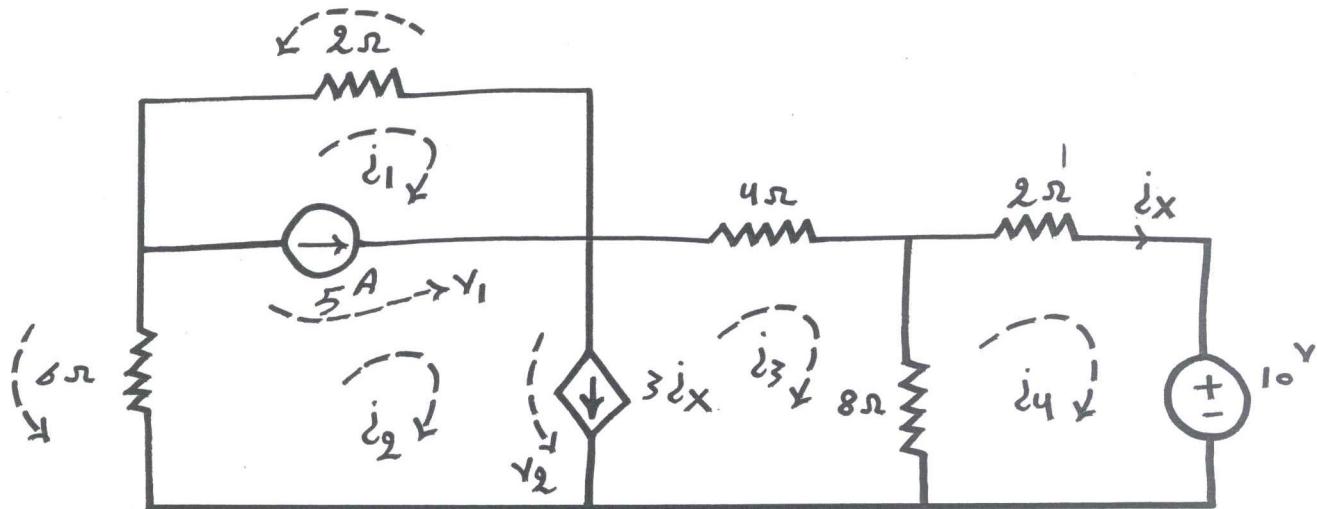**Example** →

10

→ Solve the previous problem using  
mesh analysis :



←--- **Solution** ---→

mesh (4)

$$\therefore 10j_4 - 8j_3 = -10$$

∴  $-8j_3 + 10j_4 = -10 \rightarrow 1$

5A current source

$$\therefore j_2 - j_1 = 5$$

∴  $-j_1 + j_2 = 5 \rightarrow 2$

II

$3 j_x^A$  current source

$$\therefore j_2 - j_3 = 3 j_x$$

$\hookrightarrow j_x = j_4$

$$\therefore j_2 - j_3 - 3 j_4 = 0 \longrightarrow \Sigma 3$$

supermesh equation

$\hookrightarrow \underline{\text{mesh } (1)} + \underline{\text{mesh } (2)} + \underline{\text{mesh } (3)} :$

$$\therefore 2 j_1 + 6 j_2 + 12 j_3 - 8 j_4 = 0 \longrightarrow \Sigma 4$$

From  $\Sigma 2$

$$\therefore j_1 = j_2 - 5$$

$\hookrightarrow \underline{\text{Sub}} \quad \underline{\text{in}} \quad \underline{\Sigma 4} :$

$$\therefore 2(j_2 - 5) + 6 j_2 + 12 j_3 - 8 j_4 = 0$$

$$\therefore 2 j_2 - 10 + 6 j_2 + 12 j_3 - 8 j_4 = 0$$

$$\therefore 8 j_2 + 12 j_3 - 8 j_4 = 10 \longrightarrow \Sigma 5$$

12

solving 1, 3 and 5

$$\therefore i_2 = -\frac{25}{82} A$$

$$\therefore i_3 = \frac{65}{82} A$$


$$\therefore i_4 = -\frac{15}{41} A \quad \rightarrow \quad i_X = i_4 = -\frac{15}{41} A$$

$$\hookrightarrow \therefore i_1 = i_2 - 5$$

$$= -\frac{25}{82} - 5 = -\frac{435}{82} A = -5.3 A$$

Now find the Power of each source:

10 V source

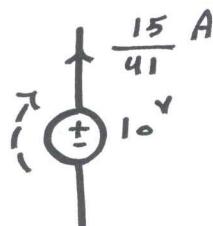

$$\therefore P_{10V} = 10 V * \frac{15}{41} A = \frac{150}{41} W = 3.66 W$$

Generated Power

5 A source

KVL at mesh 1:

$$\therefore v_1 = -2 i_1 = -2 \left( -\frac{435}{82} \right)$$

$$\therefore v_1 = \frac{435}{41} V = 10.61 V$$

$$\therefore P_{5A} = 5^A \times \frac{435}{41} V$$

$$\therefore P_{5A} = \frac{2175}{41} W = 53.049 W$$


Generated Power

$\exists i_x$  Source

→ KVL at mesh (2):

$$\therefore V_1 + V_2 - 6i_2 = 0$$
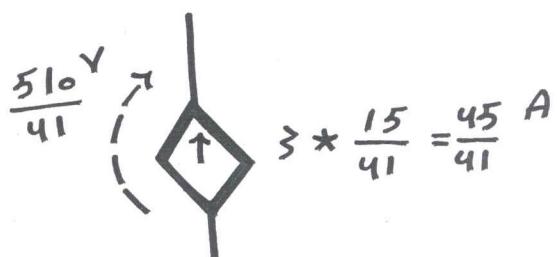
$$\begin{aligned}\therefore V_2 &= 6i_2 - V_1 \\ &= 6\left(-\frac{25}{82}\right) - \frac{435}{41} \\ &= -\frac{510}{41} V\end{aligned}$$



$$\therefore P_{\exists i_x} = \frac{510}{41} V \times \frac{45}{41} A$$


$$\therefore P_{\exists i_x} = 13.65 W$$

Generated Power

→ check Power balance to verify your answer.

Final (2016) →

→ For the shown circuit:

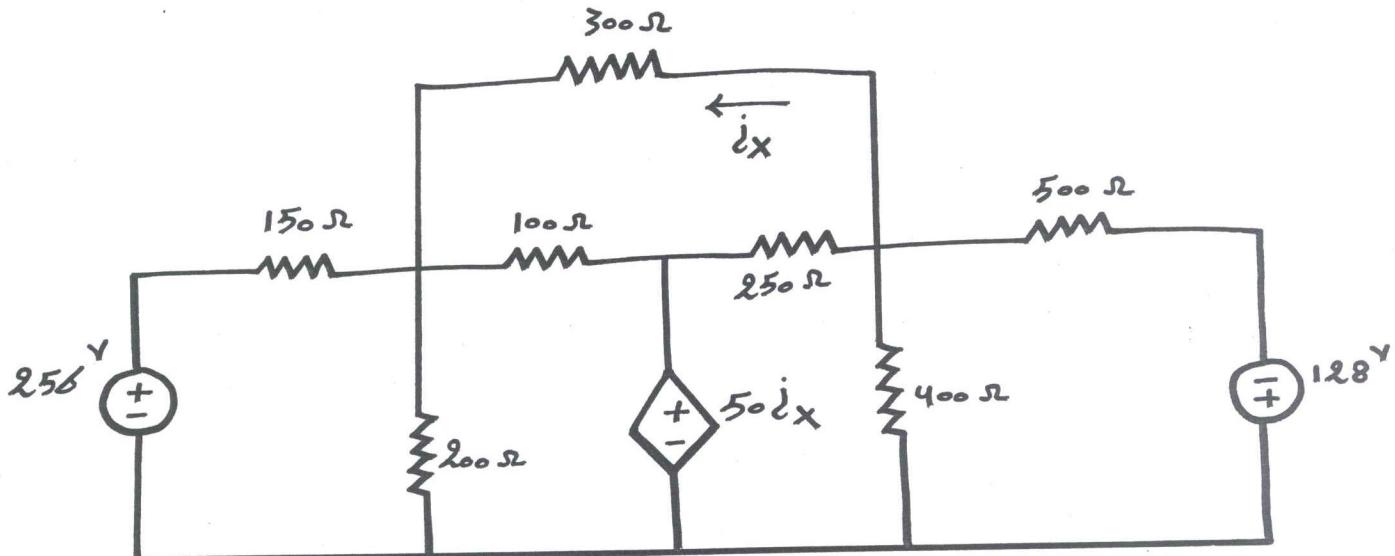

(a) Is it better to use nodal analysis or mesh analysis to solve this circuit? Give detailed reasons to your answer.

(choice)

(b) Based on your preference in Part (a), solve the shown circuit and find the value of the dependent voltage source  $50jx$ .

(c) Find the power of each source in this circuit and state whether this power is supplied or consumed by the source.

← ----- Solution ----- →


(a)

↳ using nodal analysis is better to solve this circuit because we have many voltage sources in this circuit and by selecting suitable reference node, the voltage at many nodes will be known and we will have only two unknowns.

↳ using mesh analysis is a bad choice because we will have 5 unknowns for the 5 meshes so we will have 5 equations to solve.

(b)

↳ using nodal analysis:

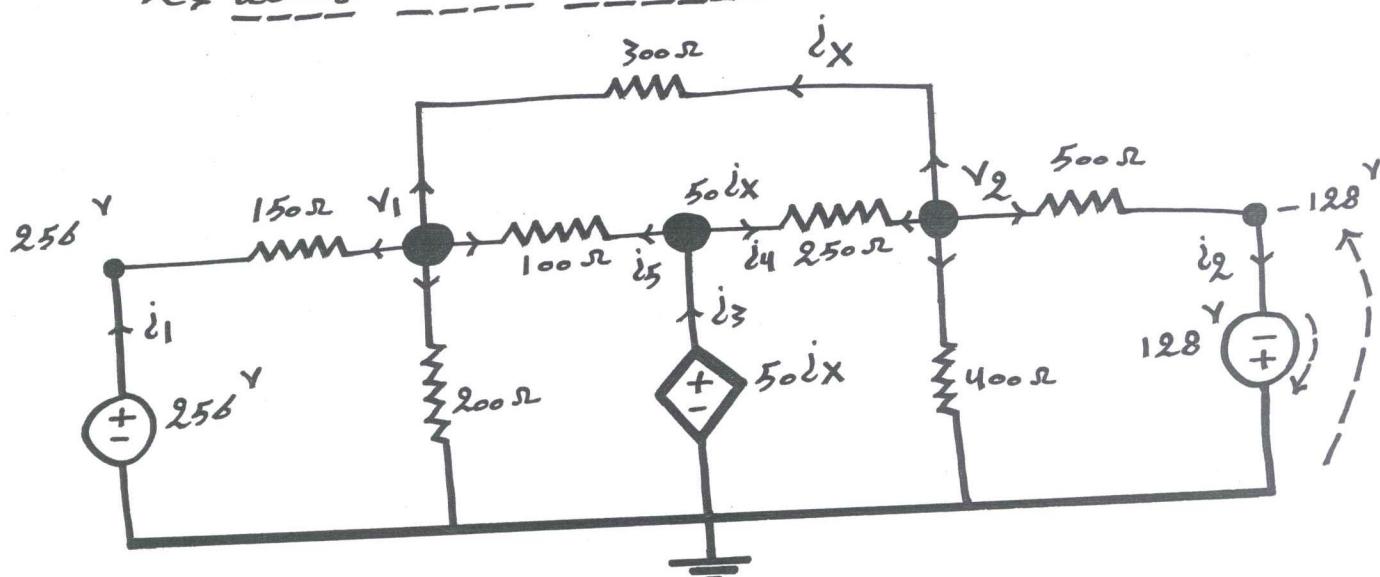

16

### KCL at node (1)

$$\therefore \frac{v_1 - 256}{150} + \frac{v_1 - 50j_x}{100} + \frac{v_1 - v_2}{300} + \frac{v_1}{200} = 0$$

$\therefore j_x = \frac{v_2 - v_1}{300}$

$$\therefore v_1 \left( \frac{1}{150} + \frac{1}{100} + \frac{1}{300} + \frac{1}{200} \right) - \frac{1}{2} j_x - \frac{1}{300} v_2 = \frac{256}{150}$$

$$\therefore v_1 \left( \frac{1}{40} \right) - \frac{1}{300} v_2 - \frac{1}{600} v_2 + \frac{1}{600} v_1 = \frac{256}{150}$$

$$\therefore v_1 \left( \frac{1}{40} + \frac{1}{600} \right) - \left( \frac{1}{300} + \frac{1}{600} \right) v_2 = \frac{256}{150}$$

$$\therefore \frac{2}{75} v_1 - \frac{1}{200} v_2 = \frac{256}{150} \quad * 300$$

$\therefore 8 v_1 - 1.5 v_2 = 512 \rightarrow ①$

### KCL at node (2)

$$\therefore \frac{v_2 - v_1}{300} + \frac{v_2 - 50j_x}{250} + \frac{v_2 + 128}{500} + \frac{v_2}{400} = 0$$

$$\therefore v_2 \left( \frac{1}{300} + \frac{1}{250} + \frac{1}{500} + \frac{1}{400} \right) - \frac{1}{300} v_1 - \frac{1}{5} j_x = -\frac{128}{500}$$

$\therefore j_x = \frac{1}{300} v_2 - \frac{1}{300} v_1$

$$\therefore \frac{1}{5} j_x = \frac{1}{1500} v_2 - \frac{1}{1500} v_1$$

17

$$\therefore \frac{71}{6000} V_2 - \frac{1}{300} V_1 - \frac{1}{1500} V_2 + \frac{1}{1500} V_1 = -\frac{128}{500}$$

$$\therefore -\frac{1}{375} V_1 + \frac{67}{6000} V_2 = -\frac{128}{500} * 6000$$

$\therefore -16 V_1 + 67 V_2 = -1536 \rightarrow 2$

Solving 1 and 2

$$\therefore V_1 = 62.5 V$$

$$\therefore V_2 = -8 V$$

$$\therefore i_x = \frac{V_2 - V_1}{300} = \frac{-8 - 62.5}{300} = -0.235 A$$

$$\therefore \text{dependent voltage source} = 50 i_x$$

$$= 50 (-0.235)$$

$$= -11.75 V$$

(c)

$$\therefore i_1 = \frac{256 - V_1}{150} = \frac{256 - 62.5}{150} = 1.29 A$$

$$\therefore \frac{P}{256 V} = 256 V * 1.29 A = 330.24 W$$

supplied Power

$$\hookrightarrow i_2 = \frac{v_2 + 128}{500} = \frac{-8 + 128}{500} = 0.24^A$$

$$\hookrightarrow \therefore P = \frac{128}{128} V \times 0.24^A = 30.72^W$$

Supplied Power

$$\hookrightarrow i_3 = i_4 + i_5$$

$$= \frac{-11.75 + 8}{250} + \frac{-11.75 - 62.5}{100}$$

$$= -0.015 - 0.7425 = -0.7575^A$$

$$\hookrightarrow \therefore P = \frac{(11.75)(0.7575)}{50} = 8.9^W$$

Supplied Power

---

**Example**

13

2.55 Find  $I_o$  in the network in Fig. P2.55.


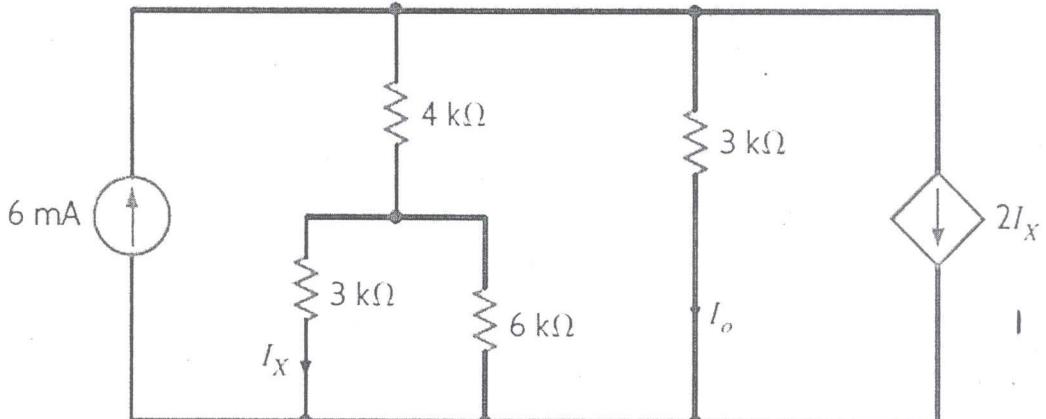


Figure P2.55

**Solution**

assumed

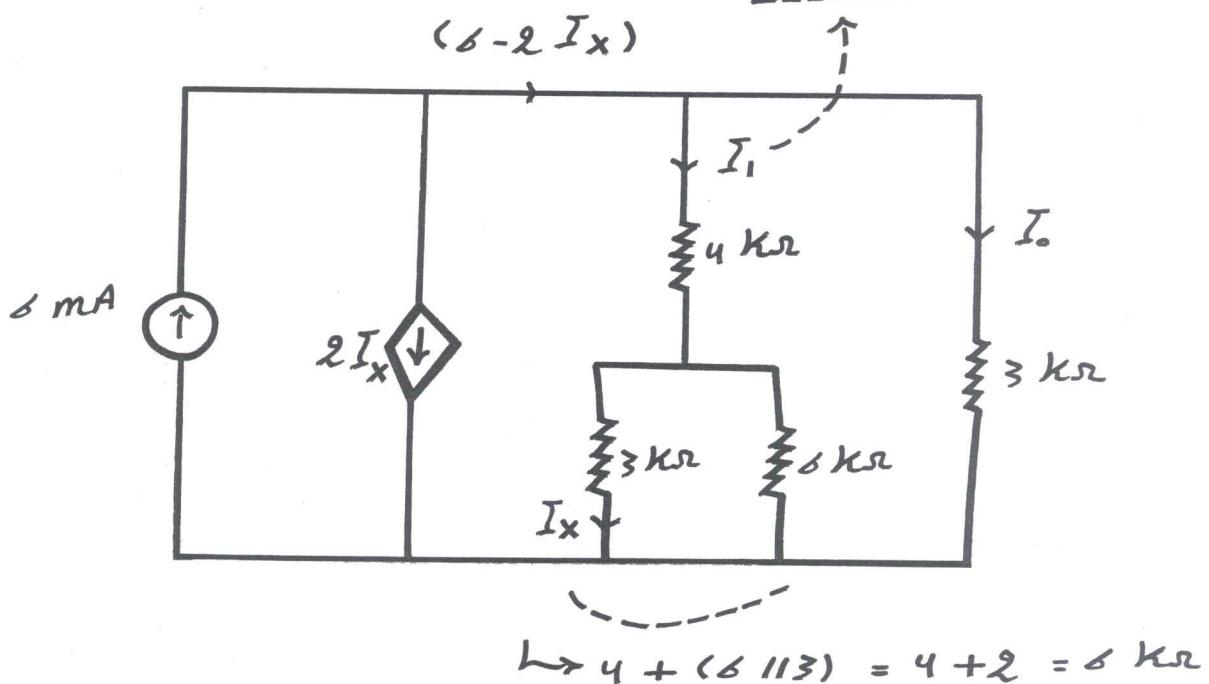

$$\hookrightarrow 4 + (6/13) = 4 + 2 = 6 \text{ k}\Omega$$

↳ current divider:

$$\therefore I_x = I_1 * \frac{6}{6+3}$$

$$\therefore I_x = \frac{2}{3} I_1$$

$$\therefore I_1 = 1.5 I_x$$

1

20

current divider

$$\therefore I_1 = (6 - 2 I_x) * \frac{3}{3+6}$$

$$\therefore I_1 = (6 - 2 I_x) * \frac{1}{3}$$

$\therefore I_1 = 2 - \frac{2}{3} I_x \rightarrow 2$

From 1 and 2

$$\therefore \frac{3}{2} I_x = 2 - \frac{2}{3} I_x$$

$$\therefore \left( \frac{3}{2} + \frac{2}{3} \right) I_x = 2$$

$$\therefore I_x = \frac{12}{13} \text{ mA}$$

current divider

$$\therefore I_o = (6 - 2 I_x) * \frac{6}{6+3}$$

$$= (6 - 2 * \frac{12}{13}) * \frac{2}{3}$$

$\therefore I_o = \frac{36}{13} \text{ mA} = 2.77 \text{ mA}$

**Example** ----->

2.67 Find  $R_{AB}$  in the network in Fig. P2.67.

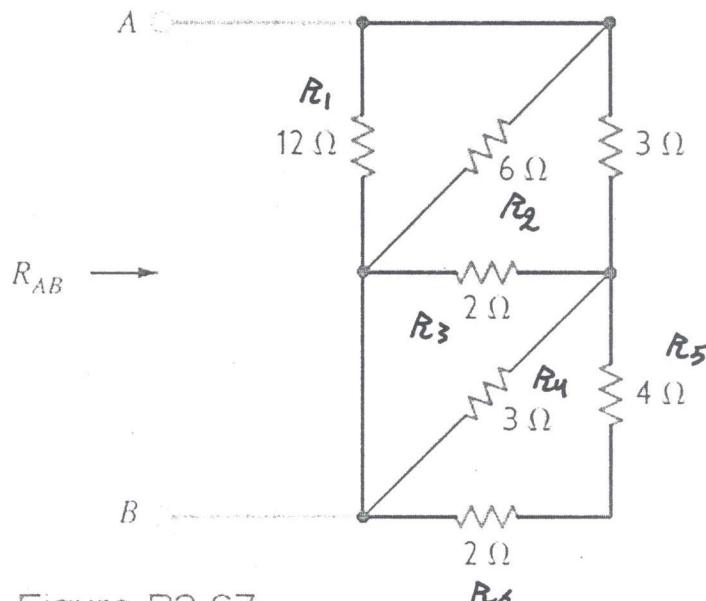



Figure P2.67

<----- **Solution** ----->

$$\hookrightarrow R_1 \parallel R_2 \longrightarrow 12 \parallel 6 = 4 \Omega$$


$$\hookrightarrow R_3 \parallel R_4 \longrightarrow 2 \parallel 3 = 1.2 \Omega$$
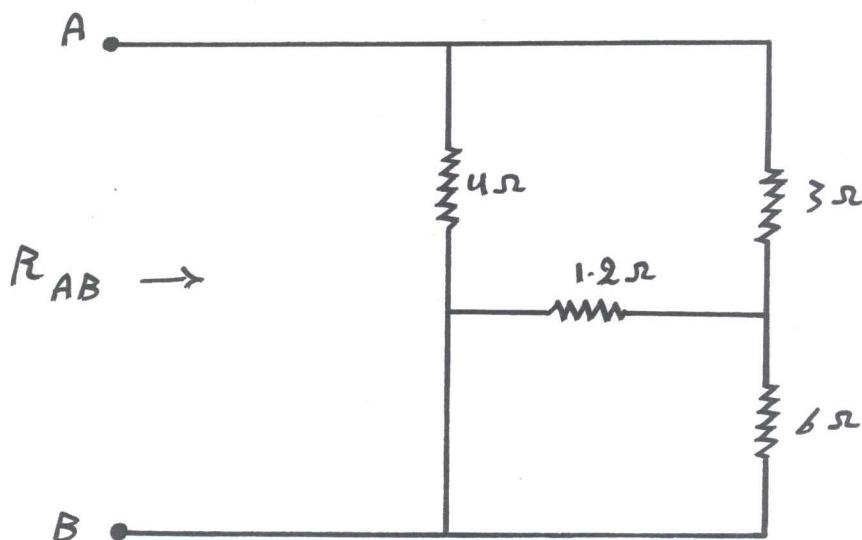
$$\hookrightarrow R_5 + R_6 \longrightarrow 4 + 2 = 6 \Omega$$



22
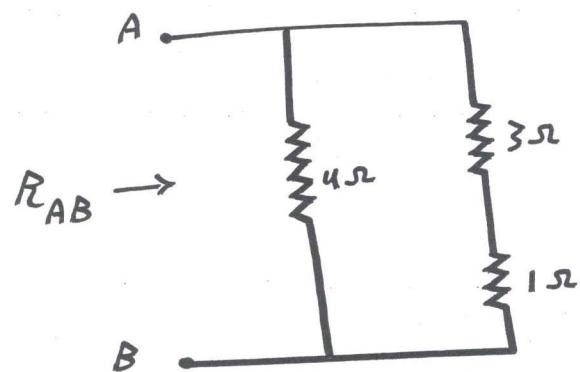
$$\text{L} \rightarrow 6 \parallel 1 \cdot 2 = 1 \Omega$$



$$\text{L} \rightarrow : R_{AB} = 4 \parallel 4$$

$$: R_{AB} = 2 \Omega$$

---

## Example →

23

2.69 Determine the total resistance,  $R_T$ , in the circuit in Fig. P2.69.

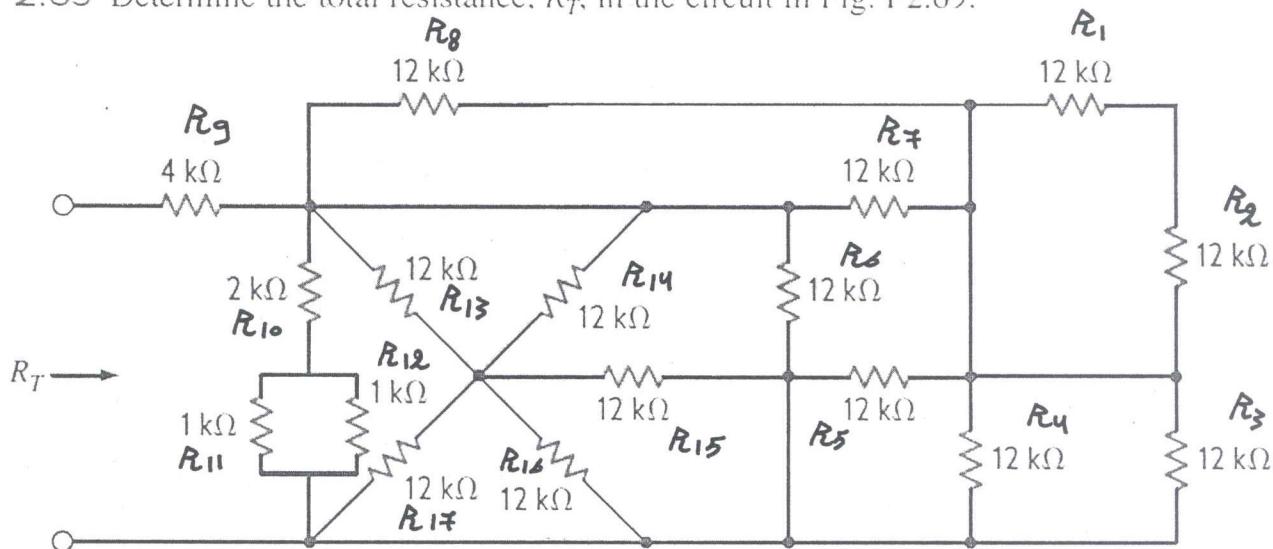


Figure P2.69

# Solution

$$\therefore R_1 + R_2 = 12 + 12 = 24 \text{ kN}$$

$$R_3 \parallel R_4 \parallel R_5 = 12 \parallel 12 \parallel 12 = \frac{12}{3} = 4 \text{ kr}$$


$$\text{L} \rightarrow R_7 \parallel R_8 = 12 \parallel 12 = 6 \text{ Ks}$$

$$L \rightarrow R_{11} \parallel R_{12} = 1 \parallel 1 = 0.5 \text{ kN}$$


$$L_7 R_{13} \parallel R_{14} = 12 \parallel 12 = 6 \text{ Ks}$$

$$\hookrightarrow R_{16} \parallel R_{17} \parallel R_{15} = 12 \parallel 12 \parallel 12 = \frac{12}{3} = 4 \text{ Ks}$$

24

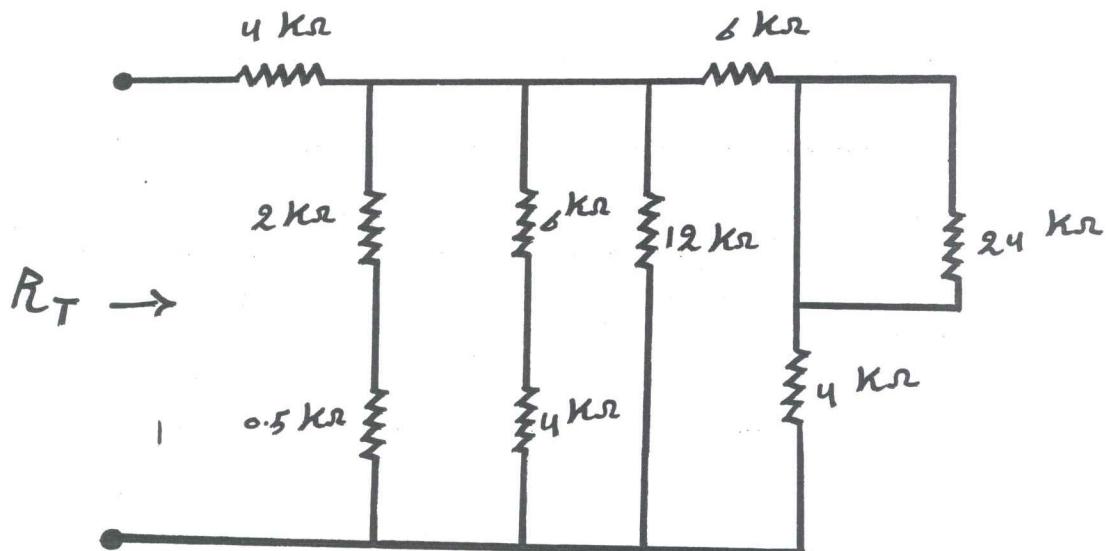

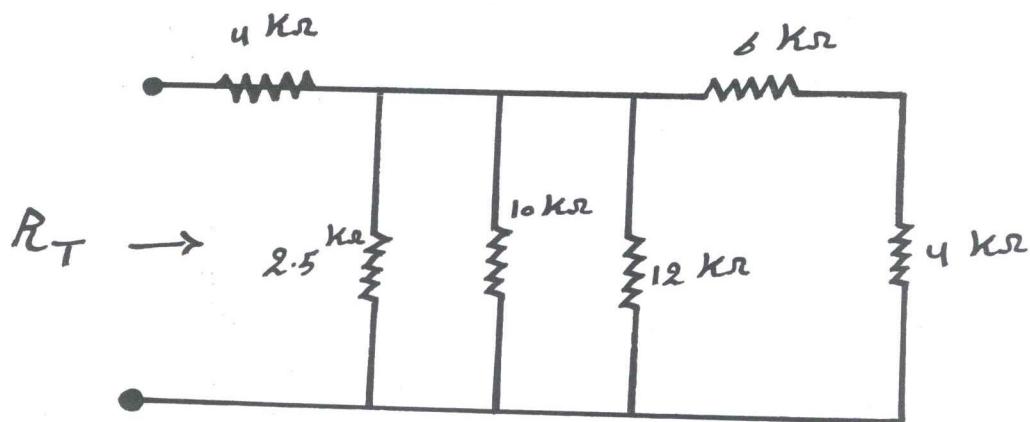$\hookrightarrow 24\text{ k}\Omega \parallel \text{ short circuit} \rightarrow \text{remove } 24\text{ k}\Omega \text{ resistor.}$



$$\therefore R_T = 4 + (2.5 \parallel 10 \parallel 10 \parallel 12)$$

$$\begin{aligned} \hookrightarrow 2.5 \parallel 10 \parallel 10 \parallel 12 &= 2.5 \parallel 12 \parallel 5 \\ &= 12 \parallel \frac{5}{3} = \frac{60}{41} \text{ k}\Omega \end{aligned}$$

$\therefore R_T = 4 + \frac{60}{41} = \frac{224}{41} \text{ k}\Omega = 5.46 \text{ k}\Omega$

# Example ----->

25

2.70 Determine the total resistance,  $R_T$ , in the circuit in Fig. P2.70.

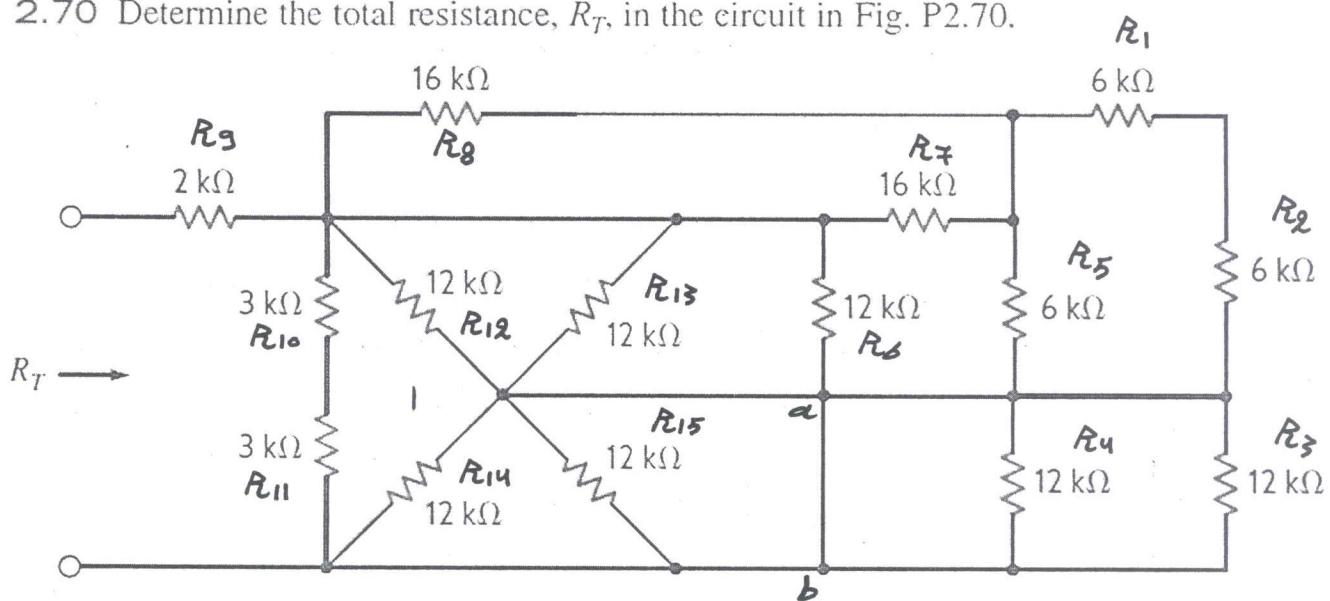


Figure P2.70

# <----- Solution ----->

$$\therefore R_1 + R_2 = 6 \text{ k}\Omega + 6 \text{ k}\Omega = 12 \text{ k}\Omega$$

$$\therefore (R_1 + R_2) \parallel R_5 = 12 \parallel 6 = 4 \text{ k}\Omega$$

$$\therefore R_7 \parallel R_8 = 16 \parallel 16 = 8 \text{ k}\Omega$$

$$\therefore R_{10} + R_{11} = 3 + 3 = 6 \text{ k}\Omega$$

$$\therefore R_{12} \parallel R_{13} = 12 \parallel 12 = 6 \text{ k}\Omega$$

$$\therefore (R_3 \parallel R_4 \parallel R_{14} \parallel R_{15}) \parallel \text{short circuit}$$

(wire ab)

$\therefore R_3, R_4, R_{14}, R_{15} \rightarrow \underline{\text{removed}}$

26

$$\begin{aligned}
 R_T &\rightarrow \\
 &2 \text{ k}\Omega \\
 &6 \text{ k}\Omega \\
 &6 \text{ k}\Omega \quad 12 \text{ k}\Omega \\
 &4 \text{ k}\Omega
 \end{aligned}$$

$$\begin{aligned}
 \therefore R_T &= 2 + (6 \parallel 6 \parallel 12 \parallel 12) \\
 &= 2 + (3 \parallel 6) \\
 &= 2 + 2
 \end{aligned}$$

$\therefore R_T = 4 \text{ k}\Omega$

# Example

27

- For the circuit shown in Fig.(1), Find  $v_0$  and  $i_0$

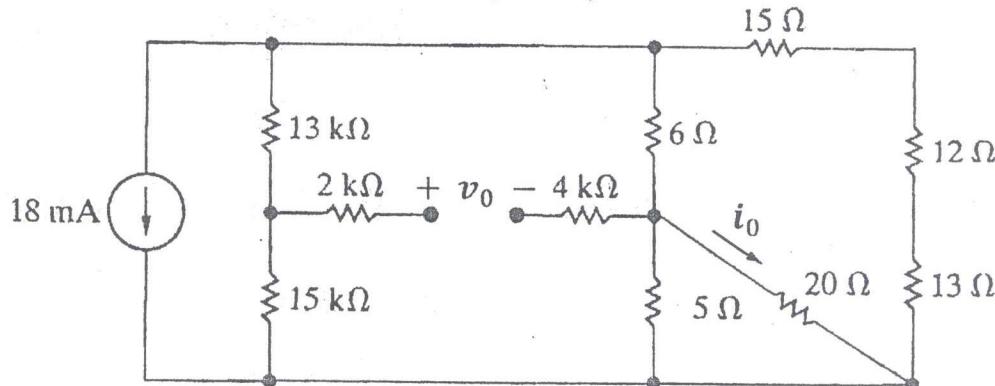


Fig.(1)


Solution

$\therefore$  current through  $2\text{ k}\Omega$  and  $4\text{ k}\Omega = \text{Zero}$

(open circuit)

$\therefore 2\text{ k}\Omega$  and  $4\text{ k}\Omega$  resistors will be removed.
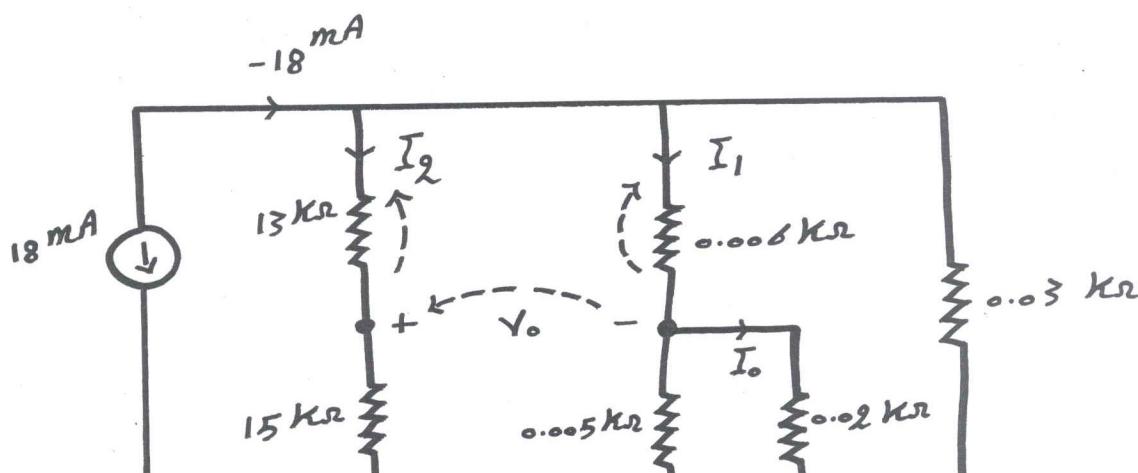
$$\therefore 15 + 12 + 13 = 30\text{ }\Omega = 0.03\text{ k}\Omega$$



$$\therefore 13\text{ k}\Omega + 15\text{ k}\Omega$$

$$= 28\text{ k}\Omega$$

$$\therefore 0.006\text{ k}\Omega + (0.005 // 0.02)$$

$$= 0.006 + 0.004$$

$$= 0.01\text{ k}\Omega$$

current divider

$$\hookrightarrow \therefore I_1 = -18 * \frac{(28 \parallel 0.03)}{(28 \parallel 0.03) + 0.01}$$

$$\therefore I_1 = -13.496 \text{ mA}$$

$$\hookrightarrow \therefore I_o = I_1 * \frac{0.005}{0.005 + 0.02}$$

$$\therefore I_o = -2.7 \text{ mA}$$

$$\hookrightarrow 0.03 \parallel 0.01 = 0.0075 \text{ k}\Omega$$

current divider

$$\hookrightarrow I_2 = -18 * \frac{0.0075}{0.0075 + 28}$$

$$\therefore I_2 = -0.0048 \text{ mA}$$


KVL

$$\therefore V_o + 13(-0.0048) - 0.006(-13.496) = 0$$

$$\therefore V_o = -0.018 \text{ V}$$


29

Example -----&gt;

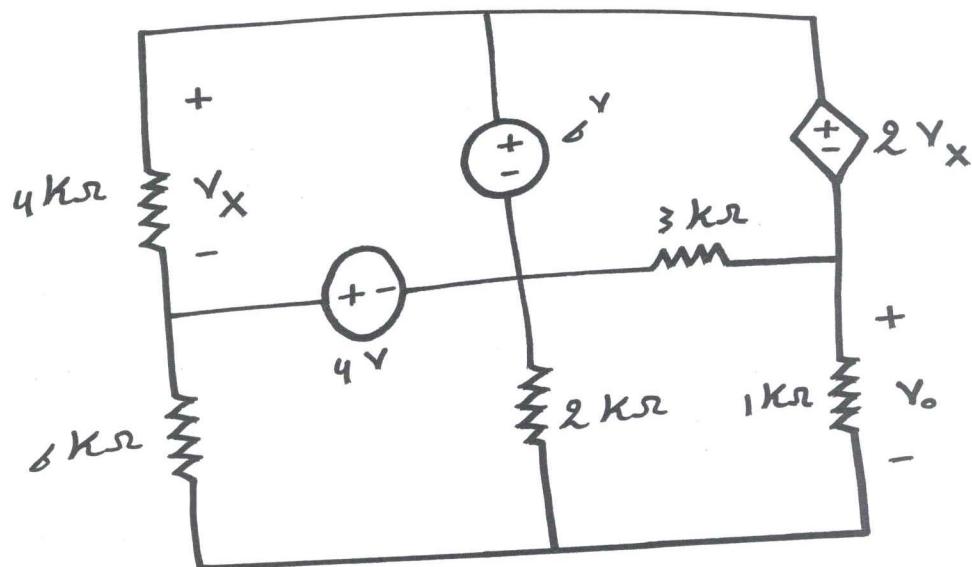-----> Find  $v_o$  using superposition.

&lt;----- Solution -----&gt;

4 V source alone

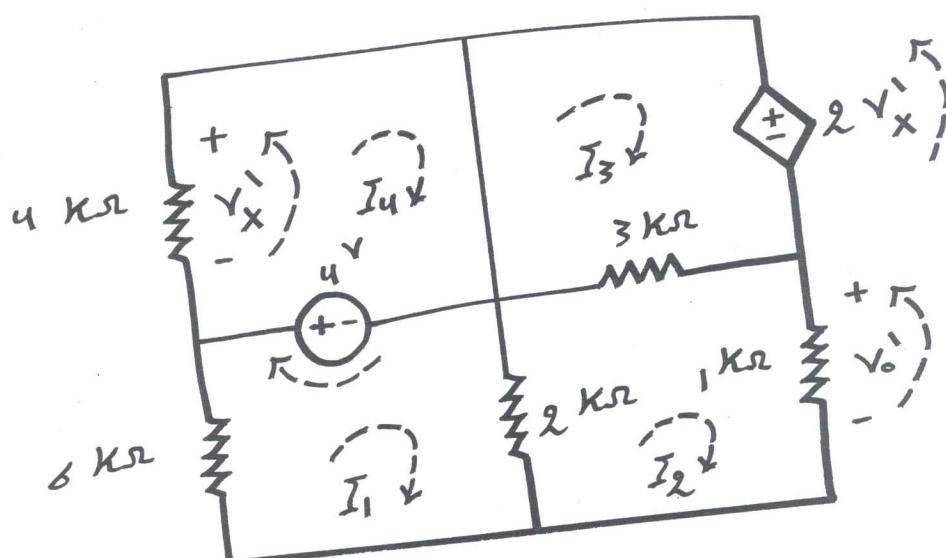

30

↳ using mesh analysis:

mesh (1)

$$\therefore 8I_1 - 2I_2 = -4 \rightarrow \textcircled{1}$$

mesh (2)

$$\therefore -2I_1 + 6I_2 - 3I_3 = 0 \rightarrow \textcircled{2}$$

mesh (3)

$$\therefore -3I_2 + 3I_3 = -2^{\vee_x}$$

↳  $v_x' = -4 \rightarrow \text{KVL at mesh (4)}$

$$\therefore -3I_2 + 3I_3 = 8 \rightarrow \textcircled{3}$$

Solving  $\textcircled{1}$ ,  $\textcircled{2}$  and  $\textcircled{3}$

$$\therefore I_1 = 0.2 \text{ mA}$$


$$\therefore I_2 = 2.8 \text{ mA} \rightarrow v_o' = (1) I_2$$

$$\therefore v_o' = 2.8^v$$

$$\therefore I_3 = \frac{82}{15} \text{ mA}$$

31

$\Sigma \delta^v$  source alone

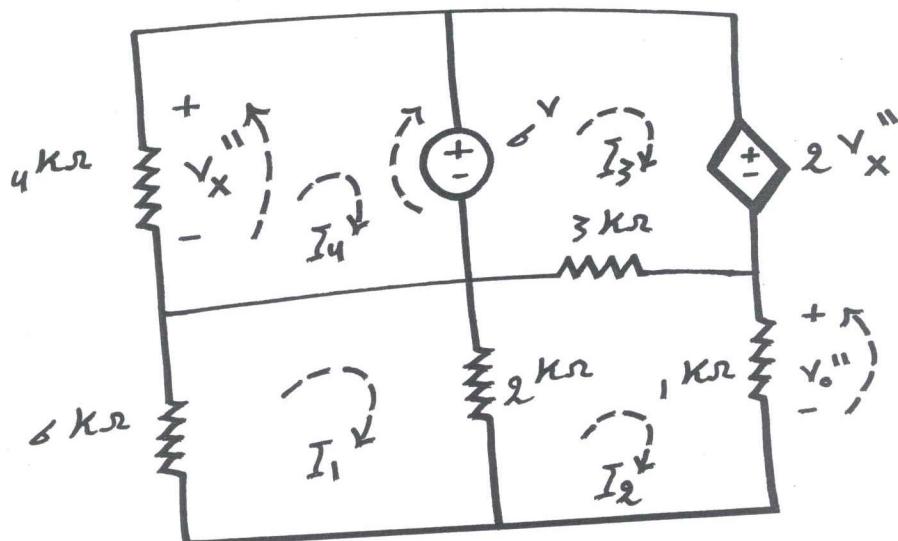

↳ using mesh analysis:

mesh (1)

$$\therefore 8I_1 - 2I_2 = 0 \rightarrow 1$$

mesh (2)

$$\therefore -2I_1 + 6I_2 - 3I_3 = 0 \rightarrow 2$$

mesh (3)

$$\therefore -3I_2 + 3I_3 = 6 - 2v_x''$$

↳  $v_x'' = \delta^v \rightarrow \underline{\text{KVL at mesh (4)}}$

32

$$\therefore -3I_2 + 3I_3 = 6 - 12$$

$$\therefore -3I_2 + 3I_3 = -6 \rightarrow 3$$

solving 1, 2 and 3

$$\therefore I_1 = -0.6 \text{ mA}$$

$$\therefore I_2 = -2.4 \text{ mA}$$

$$\therefore I_3 = -4.4 \text{ mA}$$

$$\hookrightarrow \therefore V_o'' = (1) I_2$$

$$\therefore V_o'' = -2.4$$

$$\hookrightarrow \therefore V_o = V_o' + V_o''$$

$$= 2.8 - 2.4$$

$$\therefore V_o = 0.4$$

## Example

33

- 5.2 Using linearity and the assumption that  $I_o = 1 \text{ mA}$ , find the actual value of  $I_o$  in the network use Fig. P5.2.


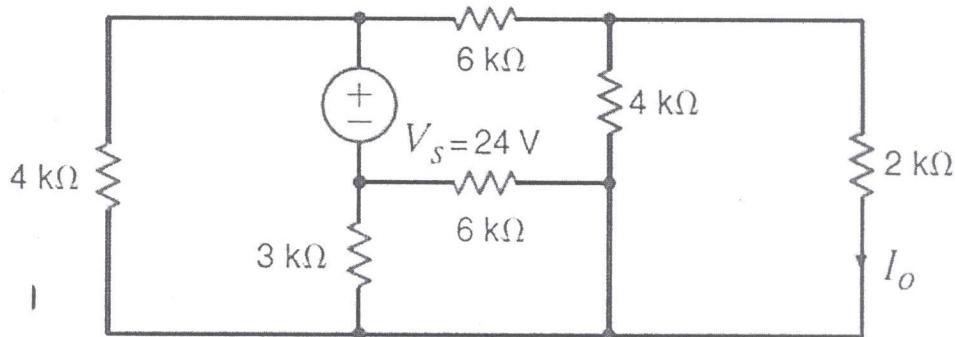


Figure P5.2

## Solution

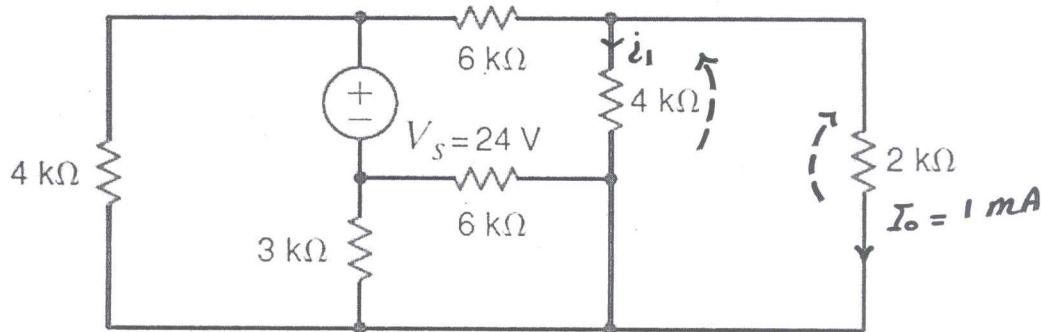


KVL

$$\text{loop } 6 \parallel 3 = 2 \text{ k}\Omega$$

$$\therefore 4i_1 = 2I_o = 2$$

$$\therefore i_1 = 0.5 \text{ mA}$$

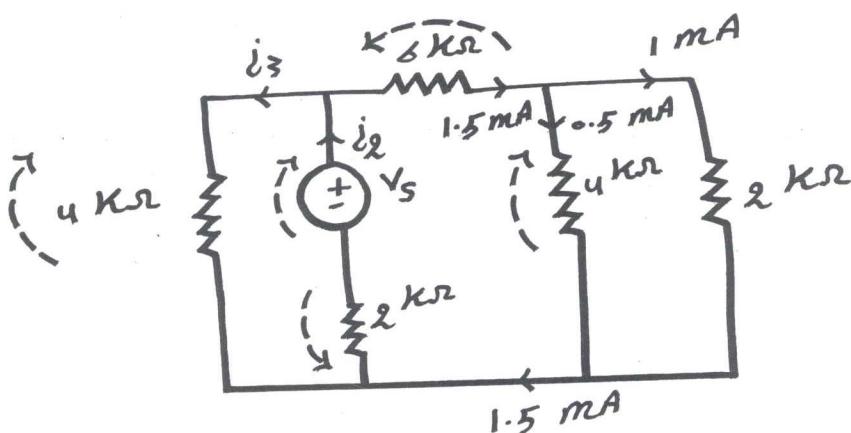

KVL

$$\therefore 4i_3 = 6(1.5) + 4(0.5)$$

$$\therefore i_3 = 2.75 \text{ mA}$$

$$\begin{aligned}\therefore i_2 &= i_3 + 1.5 \\ &= 2.75 + 1.5 \\ &= 4.25 \text{ mA}\end{aligned}$$

KVL :  $\Sigma$  Get  $V_s$  :

$$\begin{aligned}\therefore V_s &= 4 i_3 + 2 i_2 \\ &= 4(2.75) + 2(4.25)\end{aligned}$$

$$\therefore V_s = 19.5^V$$


$$\hookrightarrow \therefore 24 = \alpha * 19.5$$

$$\therefore \alpha = \frac{24}{19.5} = \frac{16}{13}$$

$$\hookrightarrow \therefore I_o = 1 \text{ mA} * \alpha$$

$$\therefore I_o = \frac{16}{13} \text{ mA} = 1.23 \text{ mA}$$


Example ----->

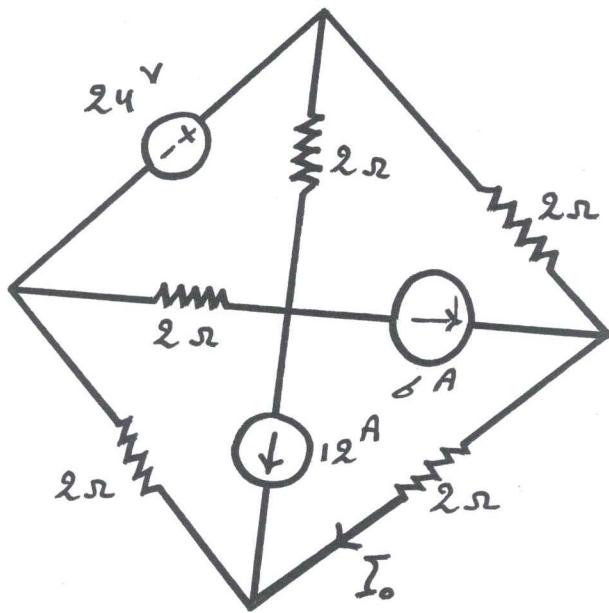

→ Find  $I_o$  using superposition theorem.

←----- Solution ----->

24V source alone

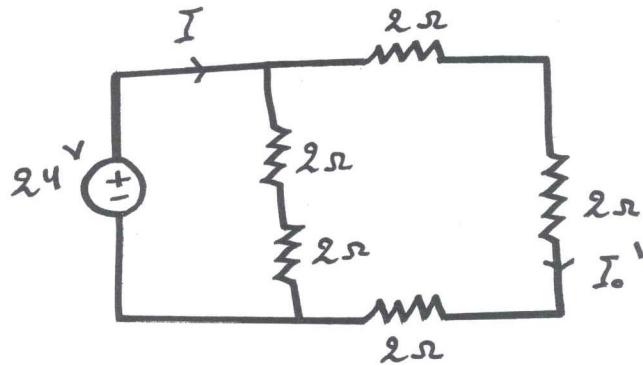

$$\therefore R_{eq} = \frac{24}{2+2+2+2} = 2.4 \Omega$$

$$\therefore I = \frac{24}{2.4} = 10 \text{ A}$$



36

## current divider

$$\therefore I_o' = 10 \times \frac{4}{4+6}$$

$\therefore I_o' = 4 \text{ A}$

$6 \text{ A}$  source alone

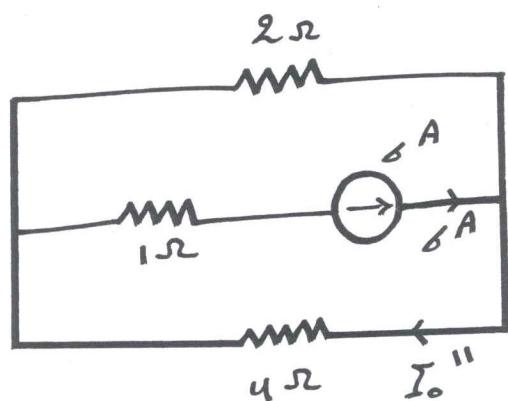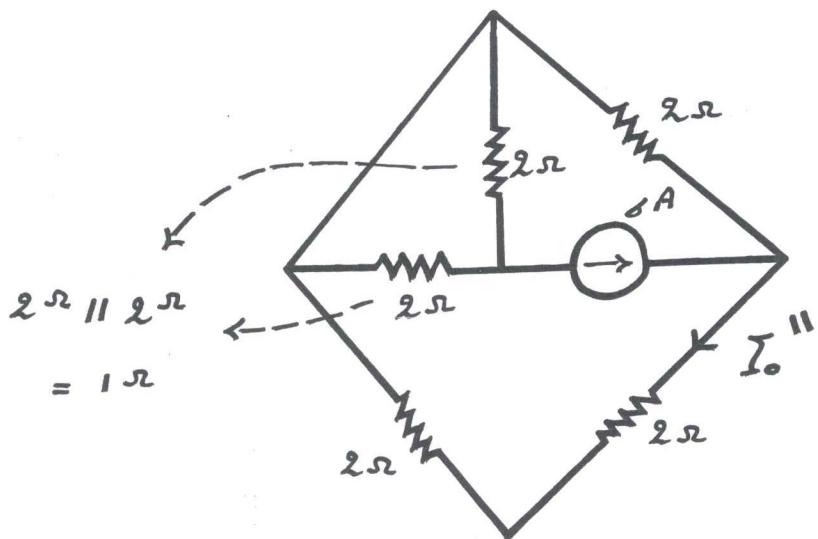



## current divider

$$\therefore I_o'' = 6 \times \frac{2}{2+4}$$

$\therefore I_o'' = 2 \text{ A}$

37

$12 \text{ A}$  source alone

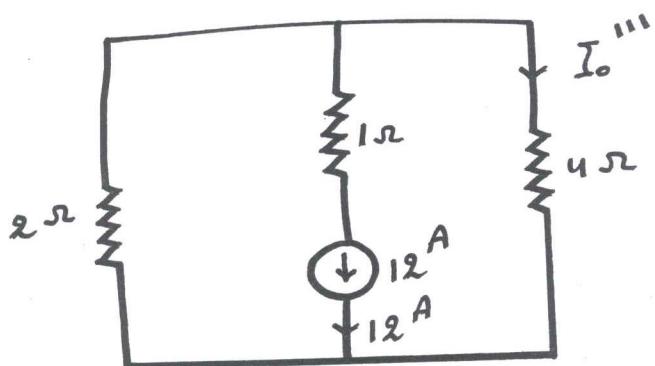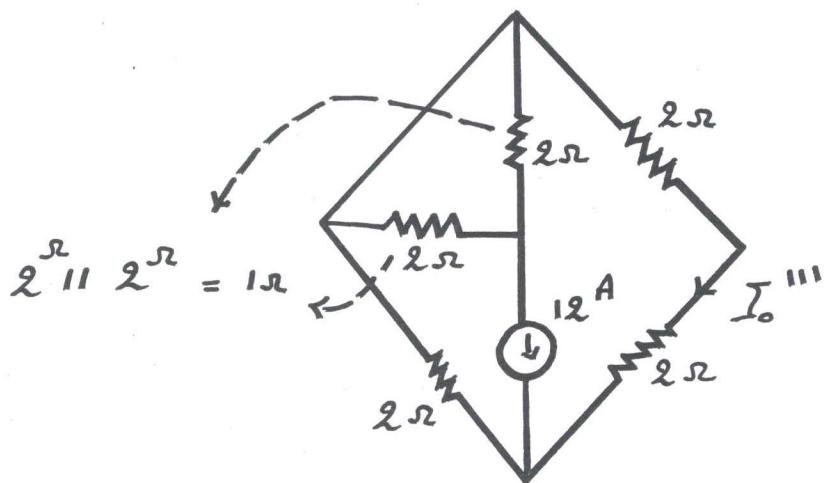

current divider

$$\therefore I_o''' = -12 \times \frac{2}{2+4}$$

$\therefore I_o''' = -4 \text{ A}$

$$\begin{aligned} \therefore I_o &= I_o' + I_o'' + I_o''' \\ &= 4 + 2 - 4 \end{aligned}$$

$\therefore I_o = 2 \text{ A}$